

Asynchronous {Pipelines, dataflow}

Honors Discussion #5

EECS 150 Spring 2010

Chris W. Fletcher

Today

- HSRA commentary
- Clocking
- Synchronizers
- Dataflow in asynchronous systems


Big Picture

- Last week: **Synchronous** pipelines
& data transactions
- This week: **Asynchronous** pipelines
& data transactions
- Next week: {Synchronous, Asynchronous} FIFOs

Clocking Basics

1


- A clock signal

 

Clocking Basics

2


- A clock signal
- Setup time

 

Clocking Basics

3

 
- A clock signal
- Setup time
- Hold time



Clocking Basics

4

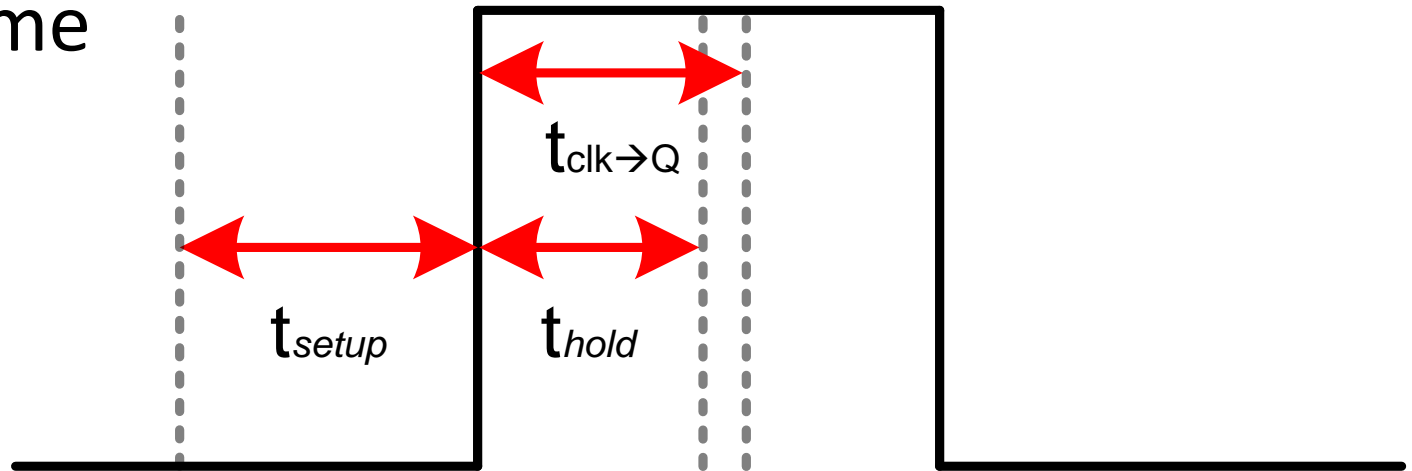- A clock signal
- Setup time
- Hold time
- $\text{clk} \rightarrow \text{Q}$




Clocking Basics

5

Quiz: Can t_{setup} or t_{hold} to be negative?

- $t_{\text{setup}} < 0$: D can change **after** the clock edge and the **new** D will be recognized
- $t_{\text{hold}} < 0$: D can change **before** the clock edge and the **old** D will be recognized

 What about $\text{clk} \rightarrow \text{Q}$?




Metastability

1

- What happens when t_{setup} or t_{hold} are violated?


- Output unknown

(somewhere between 0 and 1)

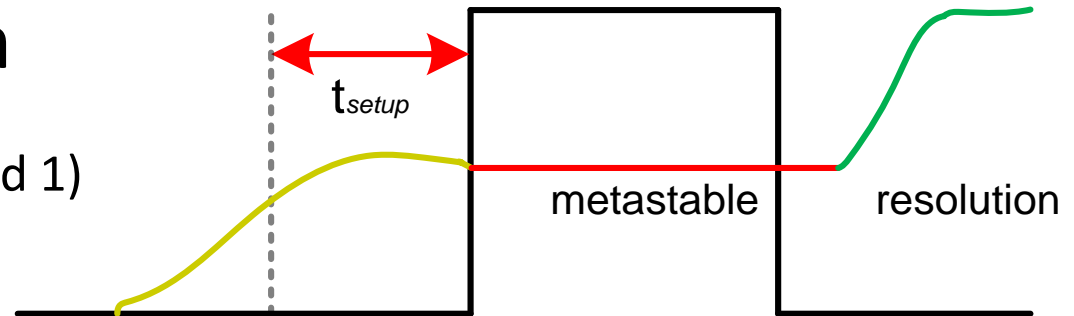

... until “resolution” occurs

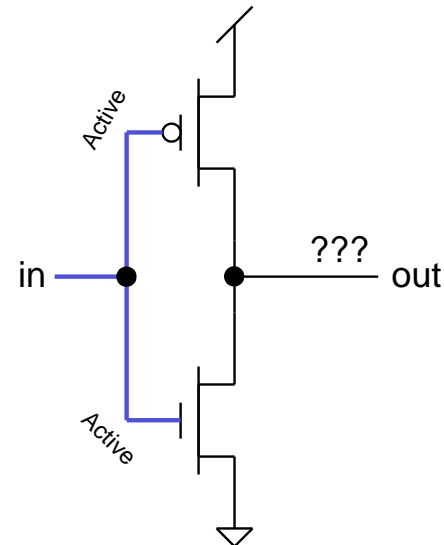at which point “out” could
be either 0 or 1!



Metastability


2

- When can t_{setup} or t_{hold} be violated?

- One Clock


Design doesn't meet timing

(You have bigger problems)

 

- Two Clocks: phase offset


May or may not cause violations

 

- Two Clocks: different frequencies

Will almost always cause violations

Thought Q: Exceptions to this?

 

Metastability


3

- Resolution must occur within t_r

$$t_r = t_p - t_{\text{clk} \rightarrow \text{Q}} - t_{\text{cl}} - t_{\text{su}}$$

- Good news:
chance to leave metastability increases exponentially with time

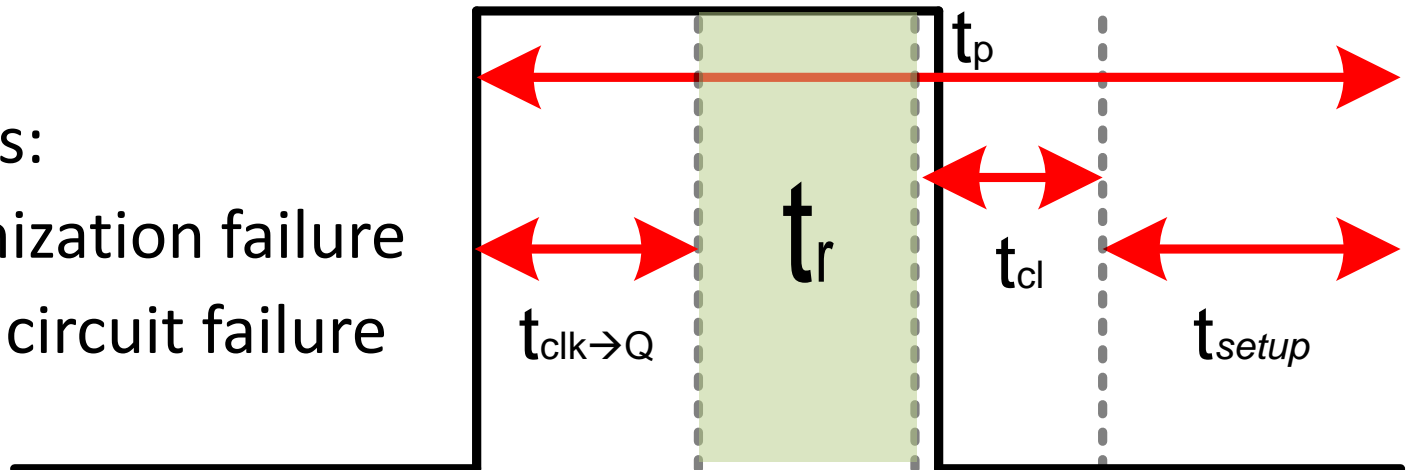
- Bad news:
synchronization failure
means... circuit failure



Synchronizers

1

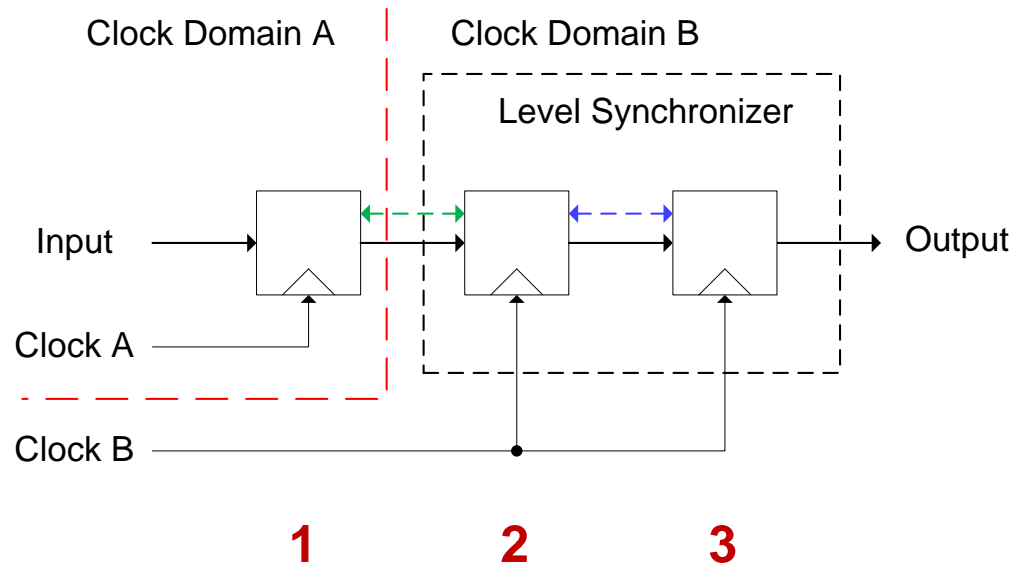- First flip-flop absorbs metastability
- Second flip-flop protects downstream logic




$$t_r = t_p - t_{\text{clk} \rightarrow Q} - t_{\text{su}}$$

Synchronizers

2

- How can we do better? Increase t_r

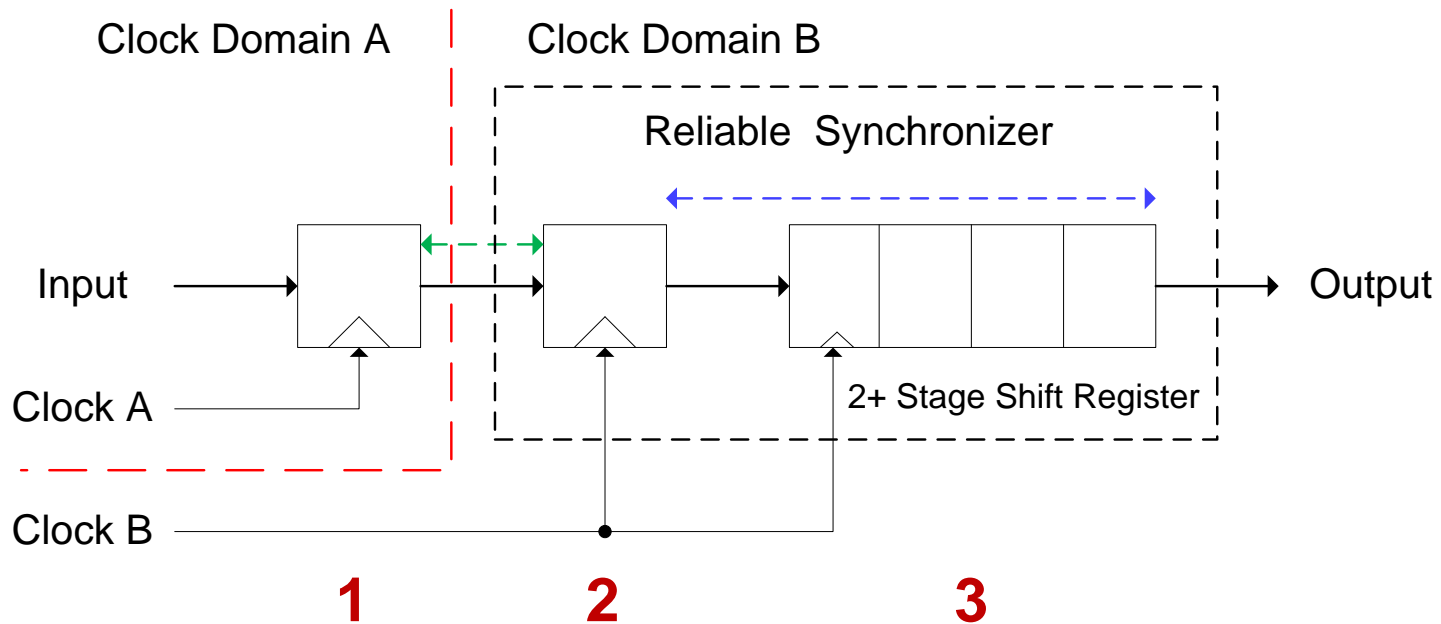


$$t_r = N \times (t_p - t_{\text{clk} \rightarrow \text{Q}} - t_{\text{su}})$$

Synchronizers

3

- Another “reliable synchronizer”

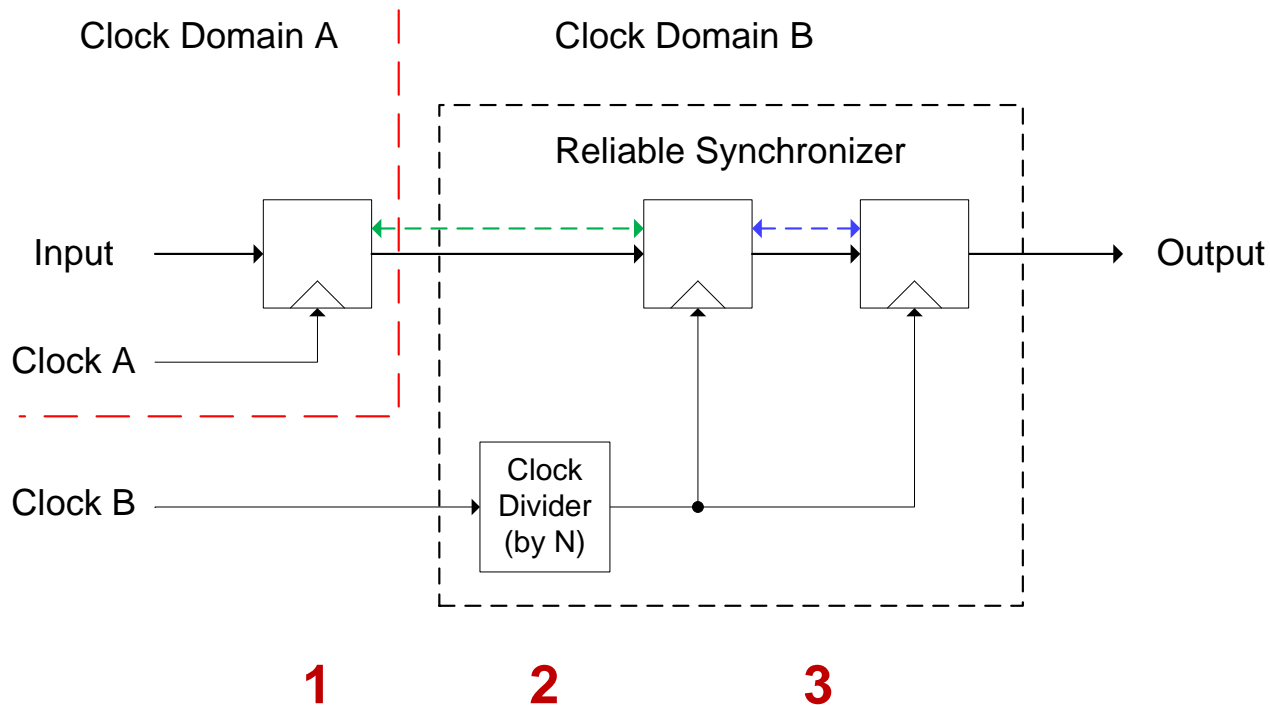

$$t_r = Nxt_p - t_{clk \rightarrow Q} - t_{su}$$

Synchronizers

4

- Synchronizer cost...
 - Area (but not much)
 - *Cycle Delay*
- Where does this matter?


Handshaking

- Case Study:
Asynchronous FIFOs

Asynchronous Pipelines


1

 - Recall... the FIFO interface that we call Ready/Valid



- This worked in a single clock domain...
- Why?

 
Transfers @ edge, both parties see change at the *same* time



Asynchronous Pipelines

2

- What happens in two clock domains?

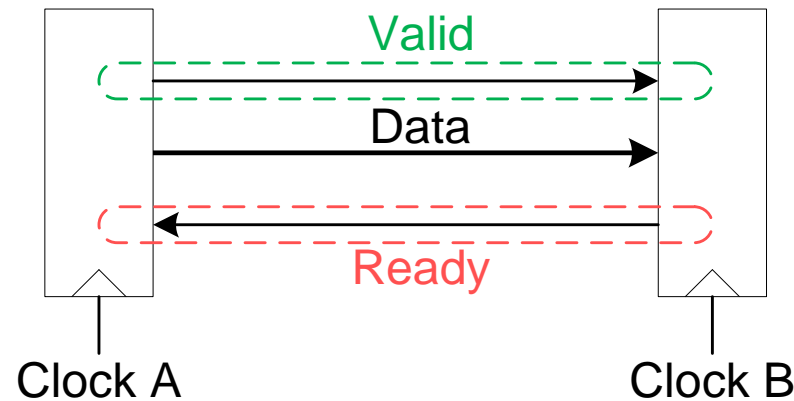


- First: we must avoid metastability. Ideas?

Asynchronous Pipelines

3

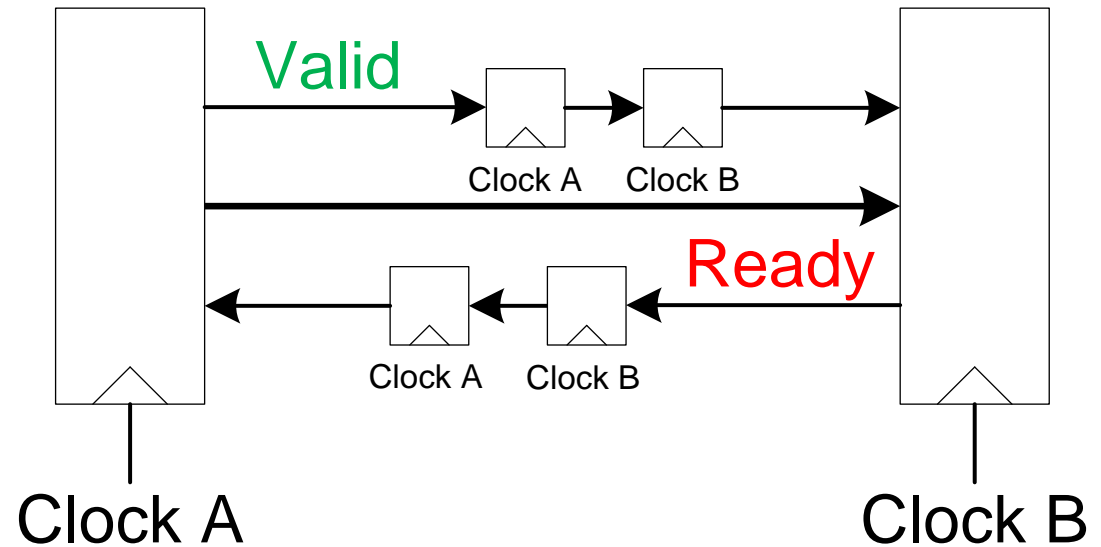- Step #1: Add synchronizers (prevents metastability)




Asynchronous Pipelines

4

- Step #1: Add synchronizers (prevents metastability)
- Step #2: Add a hold register (does this help here?)

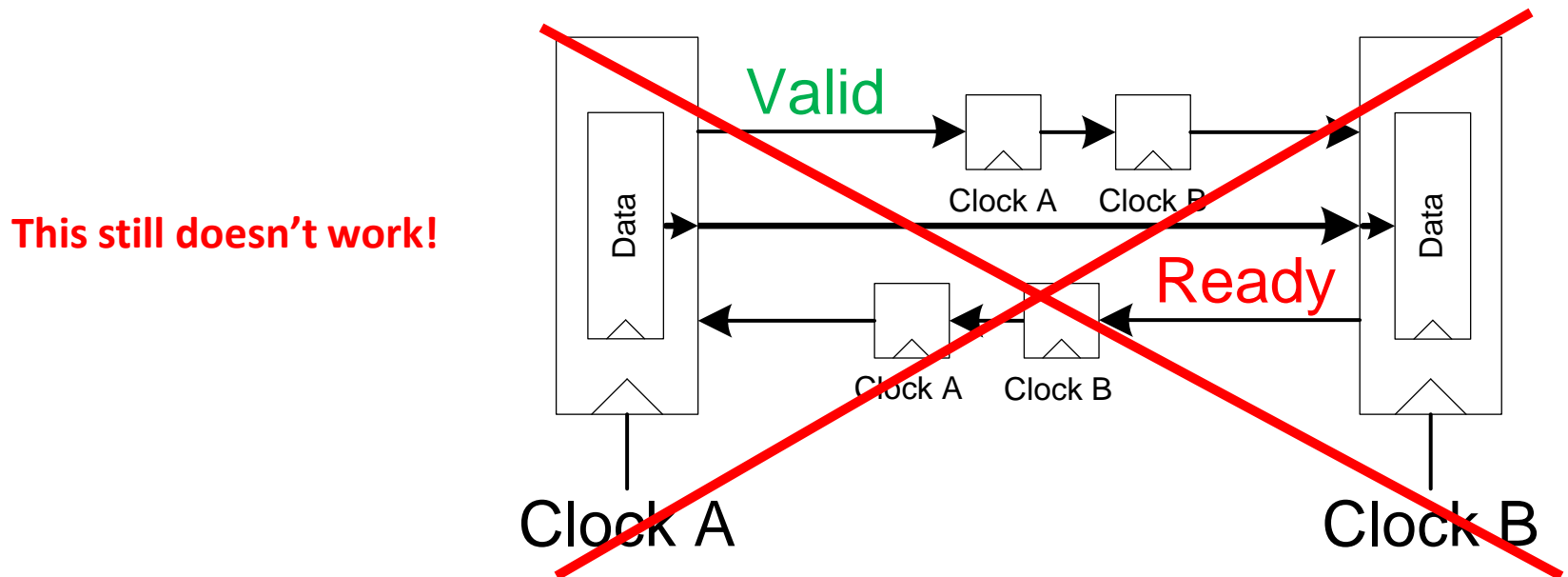Aside: Why not push data through parallel synchronizers?




Asynchronous Pipelines

5

 - Problem:
 - It takes multiple cycles for a message *from* the receiver *to reach* the sender

- Why do we care?
 - What happens when the receiver says “stop?” (i.e. DataInReady = 0)




- Solution
 - Add buffering to the receiver
 - Add “almost full” like in lecture

Asynchronous Pipelines

6

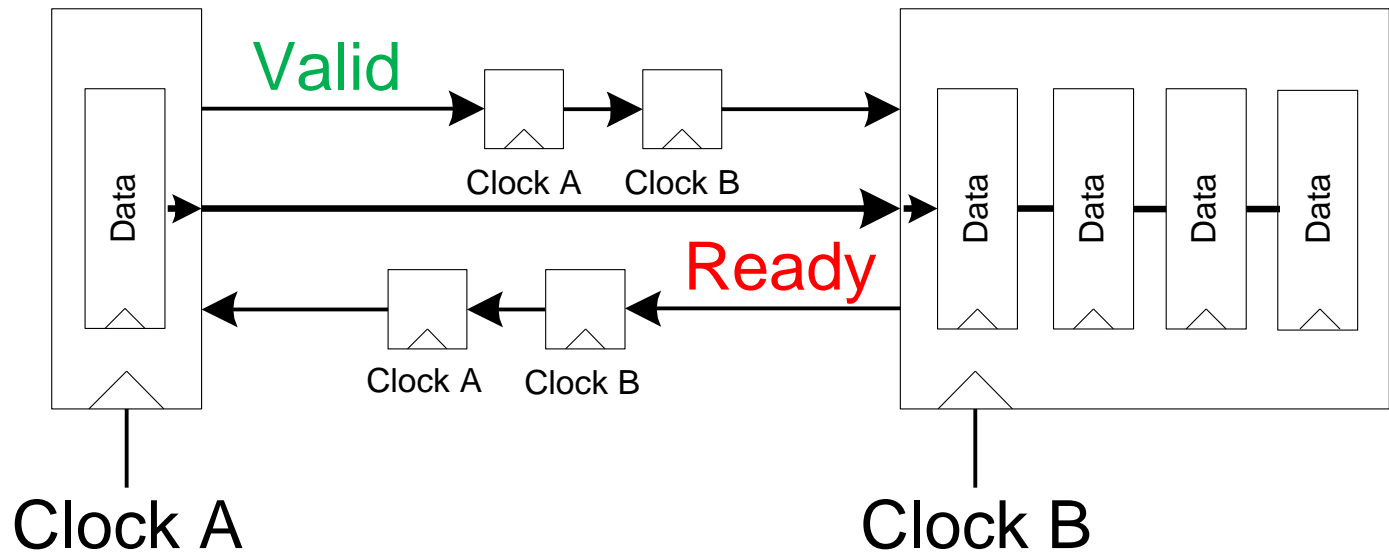- “Almost full” gives sender time to stop



- Same idea as what you saw in lecture
- What is the receiver starting to look a lot like?

Homework

- Thought problem
 - Based on what you have seen in lecture & today:
Draw a block diagram for a synchronous FIFO
 - (More) reading will be posted

Acknowledgements & Contributors

Slides developed by Chris Fletcher (2/2010).

This work is based on ideas and discussions with:

Ilia Lebedev, Greg Gibeling, John Wawrzynek, Krste Asanovic,
and other fellow Spring 2009 CS294-48 students

This work has been used by the following courses:

- UC Berkeley CS150 (Spring 2010): Components and Design Techniques for Digital Systems