

# Synchronous {Pipelines, dataflow}

Honors Discussion #4

EECS 150 Spring 2010

Chris W. Fletcher

# Today

- SCORE commentary
- Synchronous pipelines
- Throughput case study

# Big Picture


- This week: **Synchronous** pipelines  
& data transactions
- Next week: **Asynchronous** pipelines  
& data transactions
- After that: ... putting it all together...  
{Synchronous, Asynchronous} FIFOs

# Synchronous Pipelines

1


- Where do we start?

With the simple case...

 

This circuit is called a *shift register or (de)serializer*

 - If you put logic in between each stage...




You get a pipeline!

# Synchronous Pipelines
 
## 2

- When/how does this work?
  - System puts data into the pipeline
  - ... knowing that it will come out at a known time




### – Considerations

- Must know each module's "latency" (doesn't have to == 1)
- Make sure the output is ready by the time it sees the data!

# Synchronous Pipelines

3

- What happens when you want to stop?

 

(i.e. output isn't ready when the data arrives)

Train wreck!

How do we fix this?

Add control logic




# Synchronous Pipelines

4

- Monolithic/lock-step approach:

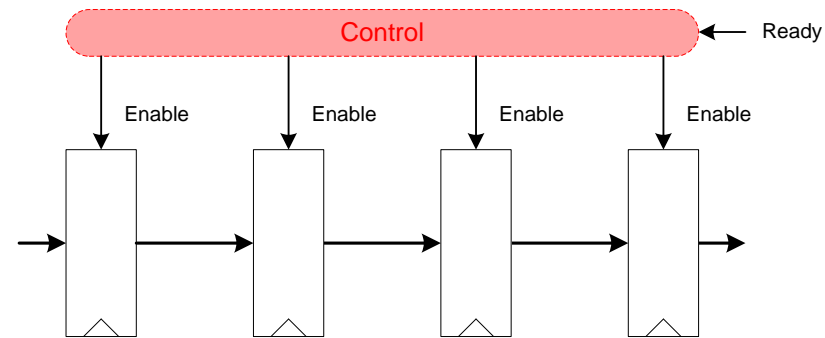
1. Controller-timed

- Controller keeps time
- **Handles 1/2+ cycle stages**



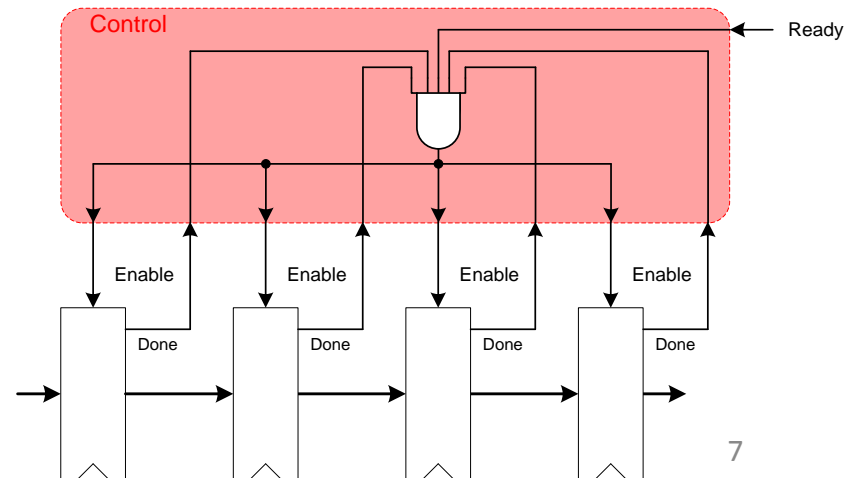1. Self-timed


- Each module keeps time
- **Handles 1/2+ cycle stages**


 
# Synchronous Pipelines

5

- Monolithic/lock-step pitfall
  - Each can handle multi-stage operations
  - But what does this do to performance?
  - Well, **NO** data moves in any stage...  
until the slowest stage is done.
  - Consider (try to find the bottleneck assuming lock-step):






# Synchronous Pipelines

6

- “Decoupled” approach

 


- No central controller
- Latency Insensitive
- Each module keeps track of its own time
- Data moves at the rate of *each* module  
**not** the rate of the slowest piece
- Sound familiar?

# Throughput Considerations

1

- A look under the covers
  - What is this register?
  - {E,R,S} match the Virtex-5
  - What events can occur?

Write	Read	Action
0	0	No change
0	1	Clear
1	0	Set
1	1	???

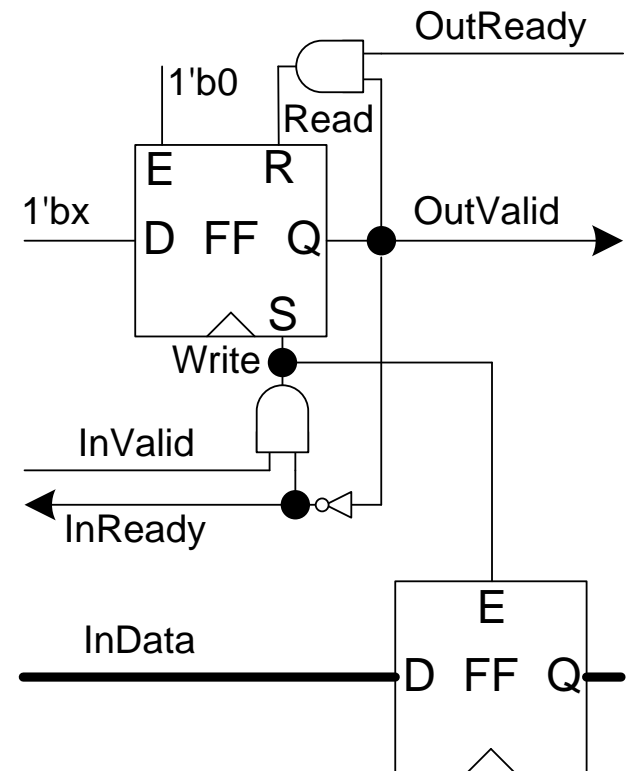

**What are the implications of this state being unreachable?**


# Throughput Considerations

## 2

- What we want: full throughput when...


Sender is constantly sending (Invalid = 1 always)

 Receiver is constantly receiving (OutReady = 1 always)



But can we ever get ideal throughput?

Write	Read	Action
0	0	No change
0	1	Clear
1	0	Set
1	1	???

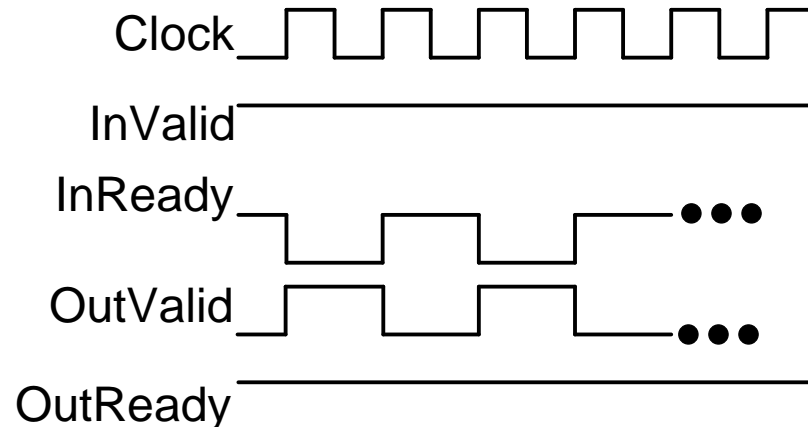

# Homework

- Thought problem
  - Fix the throughput issue  
(allow for ideal throughput)
- (More) reading will be posted

# Acknowledgements & Contributors

Slides developed by Chris Fletcher (2/2010).

This work is based in part on slides by:

Krste Asanovic, John Wawrzynek, and John Lazzaro

And is based on ideas by:

Greg Gibeling

This work has been used by the following courses:

- UC Berkeley CS150 (Spring 2010): Components and Design Techniques for Digital Systems